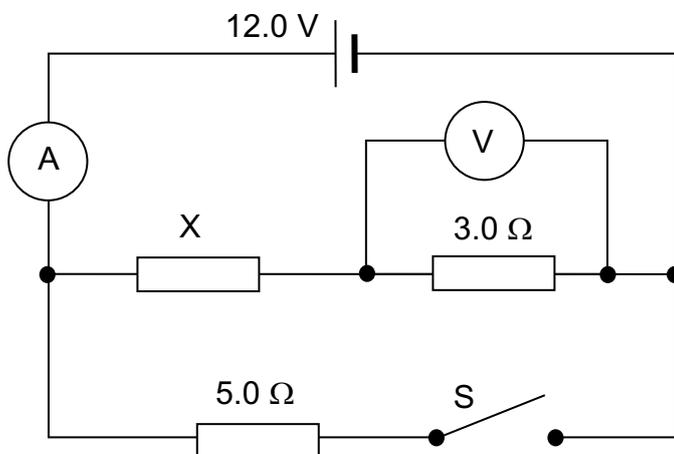


Practice Questions: Electric Circuits – 1

- 1 In the circuit shown below the resistance of the battery and the meters may be ignored. The switch S is initially **closed**.



- (a) Given that the voltmeter reads 4.0 V, calculate the value of resistor X.

resistance X = [1]

- (b) Calculate the reading on the ammeter.


ammeter reading = [2]

- (c) State the changes, if any, that would be observed on the ammeter and voltmeter when S is opened.

.....

 [1]

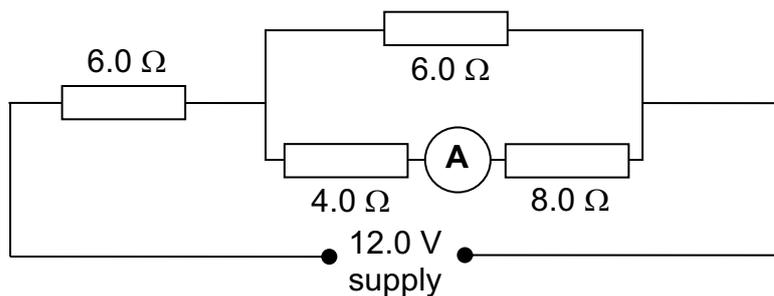- 2 Four resistors and an ammeter are connected to a 12.0 V d.c. supply as shown below:




- (a) Calculate the effective resistance of the circuit.

effective resistance = [2]

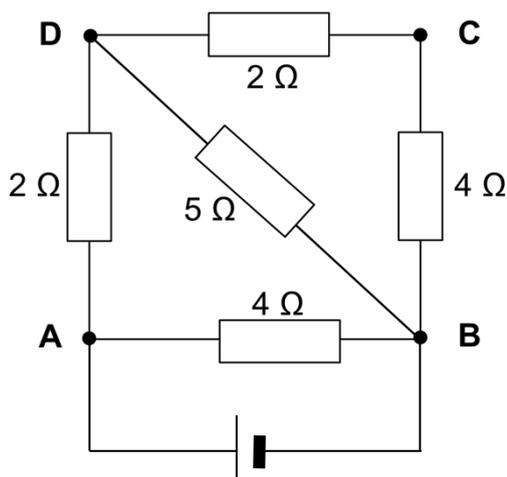- (b) Determine the reading shown on the ammeter.

reading on ammeter = [2]

- 3 Calculate the effective resistance across **AB**.



effective resistance = [2]

- 4 A lamp and a resistor are connected in series to a battery as shown in **Fig. 1**. **Fig. 2** is the characteristic graph of the lamp and the resistor which shows how the current through each component changes as the potential difference changes.

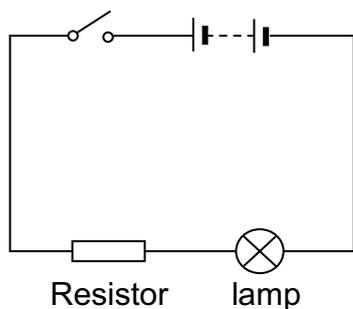


Fig. 1

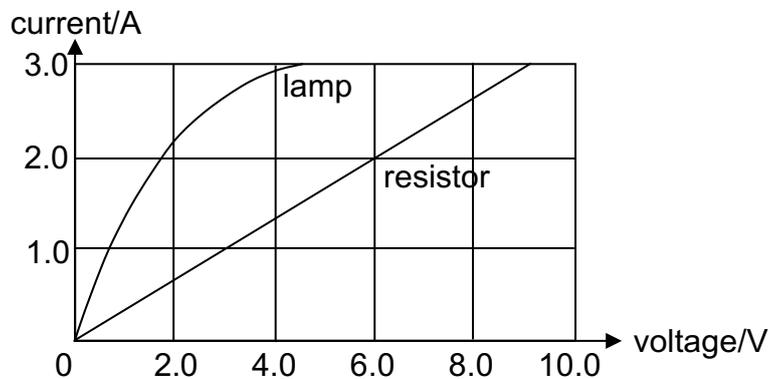


Fig. 2

- (a) State Ohm's Law.

.....

.....

.....


- (b) Describe how the resistance of the lamp changes as the potential difference increases?

.....

.....

- (c) When the circuit in **Fig. 1** is closed, the current flowing in the circuit is 3.0 A, find the potential difference across the battery.

5

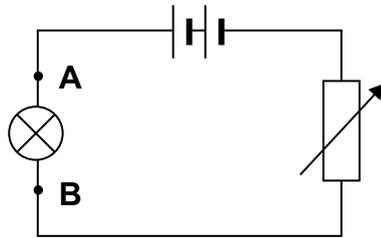

Describe the effect on the light bulb in the circuit shown 1 above if

- (a) a piece of copper wire is connected between the points **A** and **B**;

.....
.....[1]


- (b) a second identical light bulb is connected between the points **A** and **B**;

.....
.....[1]

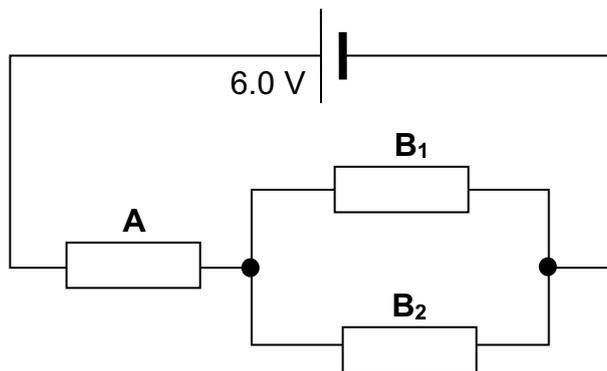- (c) one of the two cells is connected in the opposite way (its terminals are reversed).

.....
.....[1]

6 An electrical circuit is set up according to the diagram given below. Resistors **A**, **B₁** and **B₂** are identical resistors, each with 4.0Ω resistance.



- (a) A student wishes to measure the current flowing through resistor **B₂**, I_2 , and the potential difference across that same resistor, V_2 .

In the space given below, redraw the above circuit diagram to show how you would connect an ammeter and a voltmeter to measure I_2 and V_2 .

(b) Given that resistors **B**₁ and **B**₂ together have an effective resistance of 2.0 Ω,
(i) Calculate the expected value for the current flowing through resistor **A**. [1]

(ii) Hence, state the expected current flowing through resistor **B**₂. [1]

(c) Using your answers from part (b),
(i) Calculate the expected potential difference across resistor **B**₂. [1]

Hence, state the expected potential difference across

(ii) Resistor **A**. [1]

(iii) Resistor **B**₁. [1]


(d) It was found that the current *measured* flowing through resistor **A** was smaller than the expected value. Suggest a reason for this observation.

.....
..... [1]

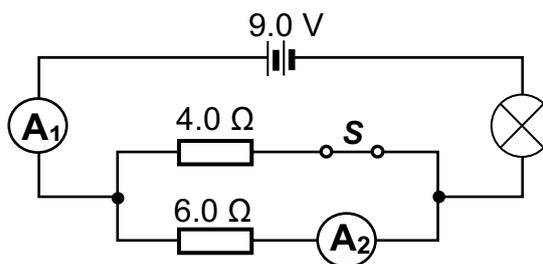(e) It was found that the potential difference *measured* across resistor **A** was **larger** than the expected value. Suggest a reason for this observation.

.....
..... [1]

- 7 In the circuit shown below, the resistance of the battery and the meters may be ignored.



The reading on ammeter A_1 is 2.5 A and the reading on A_2 is 1.0 A.

- (a) Determine the current flowing through the 4.0 Ω resistor.

current =[1]

- (b) Calculate potential difference across the 6.0 Ω resistor.

potential difference =[1]

- (c) Calculate the potential difference across the bulb.

potential difference =[1]

- (d) Suggest and explain how the brightness of the bulb will be affected when switch **S** is opened.

.....

