

ANSWERS

1

- (a) $V=IR = 0.50 \times 18.0 = \underline{9.0 \text{ V}}$
(b) Current = $0.50 + 2(0.50) = \underline{1.50 \text{ A}}$
(c) Potential difference between R and S = $(1.50 \text{ A} \times 2.0 \Omega) + 9.0 \text{ V}$
 $= 3.0 \text{ V} + 9.0 \text{ V} = \underline{12 \text{ V}}$
(d) Power = $V^2/R = 12^2/4 = \underline{36 \text{ W}}$

2

- (a) $V = IR \quad \rightarrow \quad I = V / R = (1.5 \times 3) / 18$
 $= 0.25 \text{ A}$
(b) $I = Q / t \quad \rightarrow \quad Q = I \times t = 0.25 \text{ A} \times 1 \text{ s} = 0.25 \text{ C}$

3

- (a) The resistance of constantan wire remains constant with change in temperature.
(b) When current flows through a tungsten wire, the wire is heated up and, according to Fig. 12.1, the resistance of the wire increases.
By $V = IR$, the current through the bulb decreases over time.
(c) 1000Ω
(d) When there is a fire, the temperature of the thermistor increases.

The resistance of the thermistor decreases with increasing temperature (Fig. 12.1) and its p.d. decreases.

The p.d. across the fixed resistor and the fire alarm (in parallel with the fixed resistor) increases.

When this p.d. exceeds V_0 , the fire alarm is triggered.

- (e) $V_0 = [R / (R + R_t) \times 9.0] = (2000 / (600 + 2000)) \times 9.0$
 $= (2000/2600) \times 9.0 \text{ V} = 6.923 \approx 6.9 \text{ V}$

4

a i Effective resistance of the voltmeter and X connected in parallel:

$$\frac{1}{R_e} = \frac{1}{2500\Omega} + \frac{1}{2000\Omega}$$


$$R_e = 1111 \Omega$$

$$\text{Reading of ammeter} = \frac{2.0 \text{ V}}{1111\Omega} = 1.8 \times 10^{-3} \text{ A}$$

a ii Value of X obtained = $\frac{2.0 \text{ V}}{0.0018 \text{ A}} = 1100 \Omega$ (2 s.f.)

b As the **resistance of X is close to the resistance of the voltmeter**, the current that flows through the voltmeter is not negligible.
The ammeter measures the **total current flowing through X and the voltmeter**.

c

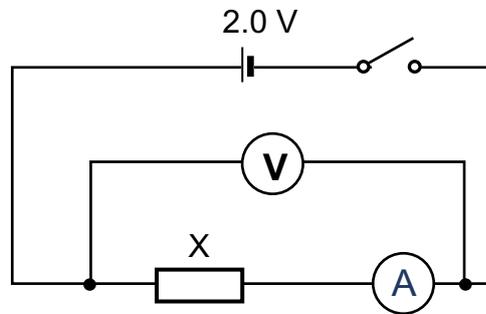

5

(a) As temperature increases, resistance of the thermistor decreases due to the increase in concentration of free mobile electrons [1].

OR

Since potential difference across the thermistor decreases as the temperature increases, it implies that the resistance of the thermistor decreases.

(b) The potential difference across the air-conditioning unit increases because the potential difference across the thermistor decreases.

(c) 30°C

(d) (i) 56 V

(ii) Current in circuit = $56/1630 = 0.034355 \text{ A}$
= 0.034 A or 34 mA (2 s.f.)

(iii) p.d. across air conditioning unit = $230 - 56 = \underline{174 \text{ V}}$

(iv) Therefore, resistance of air conditioning unit
= $174/0.034355$
= 5060 Ω (3 s.f.)

(e) At 58°C, p.d. across thermistor is 32 V (from graph)

p.d. across air conditioning unit = $230 - 32 = \underline{198 \text{ V}}$

Current through thermistor = $198/5060 = \underline{0.03913 \text{ A}}$

Therefore, resistance of thermistor = $32/0.03913 = \underline{818 \Omega}$ (3 s.f.)

6

(a) 75Ω

(b) effective resistance = $75 + 15 = 90 \Omega$

$$I = V / R = 2.0 / 90 = 0.022 \text{ A}$$

(c)

(i) Correct statement of relationship between thermistor temperature and its resistance. R increases as T decreases OR vice-versa is sufficient.

Clear indication of role of heating element to raise temperature of thermistor. Mention of either increase in current or potential difference causing the bulb to light up.

Mention of significance of the parallel arrangement – maintain constant V across the parallel branches OR use of potential divider effect in the thermistor/bulb branch.

(ii) Let the resistance of thermistor be R at the lowest temperature.

$$V = IR, \quad 2.0 = (12.1 \times 10^{-3}) \times (R + 15)$$

$$R + 15 = 165.3$$

$$R = 150.3 \Omega$$

From the graph,

temperature of the thermistor $\approx 40 \text{ }^\circ\text{C}$