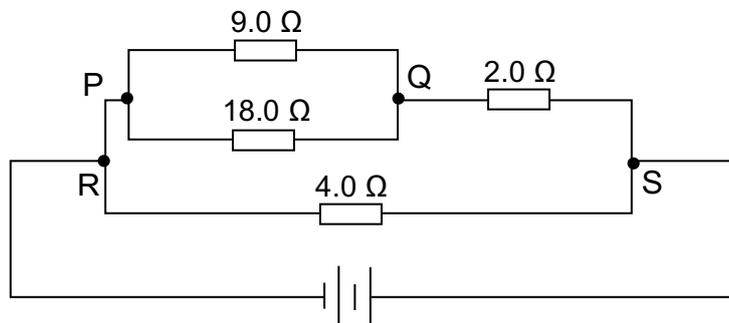


Practice Questions: Electric Circuits – 2

- 1 A circuit is shown below in which the connecting wires have negligible resistance. The current in the $18.0\ \Omega$ resistor is $0.50\ \text{A}$.



Calculate:

- (a) the potential difference between P and Q,

potential difference =[1]

- (b) the current in the $2.0\ \Omega$ resistor,

current =[1]


- (c) the potential difference between R and S,

potential difference =[2]

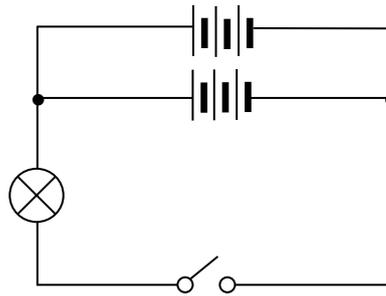- (d) the power dissipated by the $4.0\ \Omega$ resistor.

power =[2]

- 2 The diagram shows a circuit diagram of a torch using six 1.5 V cells to light a bulb with resistance 18Ω .




- (a) Calculate the current through the bulb when the torch is switched on.

current =

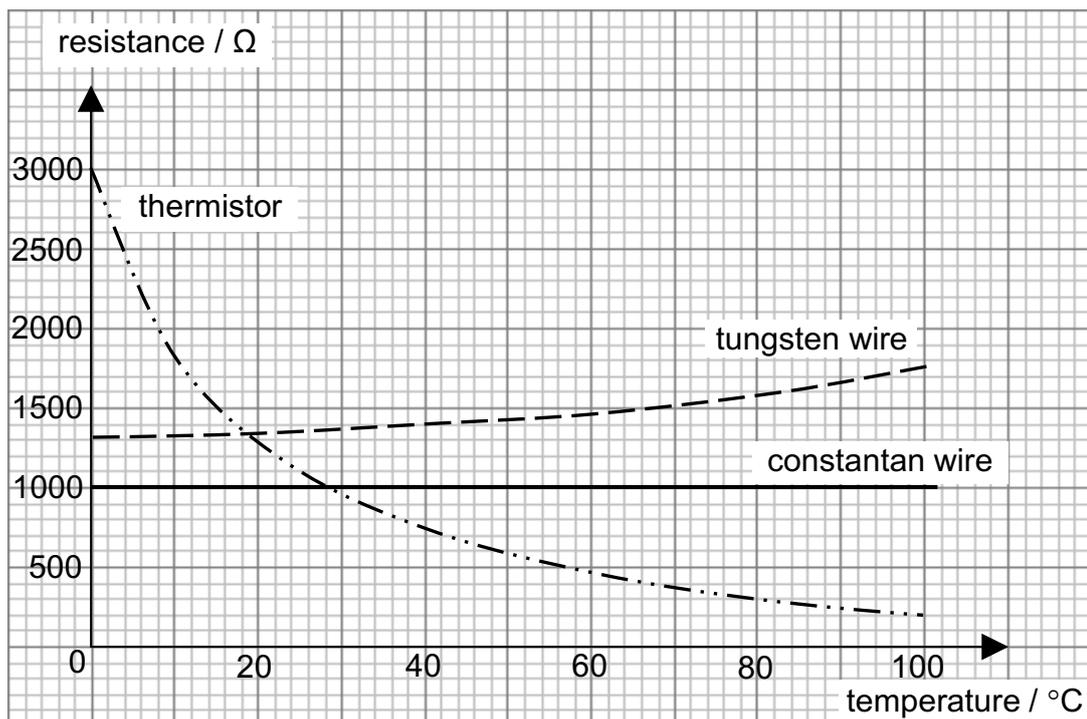- (b) Hence, calculate the amount of electrical charge passing through the bulb each second.

charge =

- 3 The graph shows how the resistance of three different circuit components changes with temperature. Constantan is an alloy of copper and nickel.



(a) Describe how the resistance of constantan changes with temperature.

.....
.....


(b) When a tungsten light bulb is switched on, describe and explain what would happen to the current passing through the light bulb over some time.

.....
.....
.....
.....

(c) State the resistance of the thermistor when the temperature is 28 °C.

resistance =

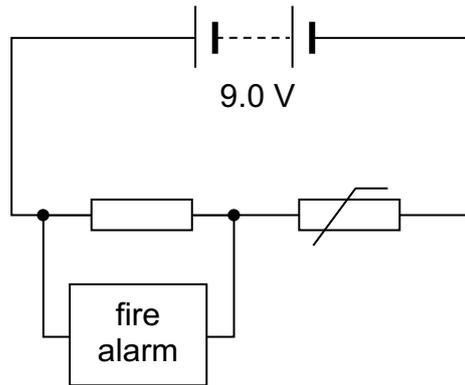(d) The thermistor can be used as a temperature sensor in a fire alarm circuit as shown below. The thermistor is connected in series with a fixed resistor and a 9.0 V battery.



The fire alarm is connected across the fixed resistor and is triggered when the potential difference across the alarm exceeds a minimum value of V_0 .

Explain clearly this application of the thermistor when there is a fire in the environment.


.....
.....
.....
.....
.....

- (e) The fixed resistor has a resistance of $2.0 \text{ k}\Omega$. When the temperature rises to $50 \text{ }^\circ\text{C}$, the resistance of the thermistor is $600 \text{ }\Omega$ and the fire alarm is just triggered.

Calculate the minimum p.d. V_o when the fire alarm is just triggered.

minimum p.d. $V_o = \dots\dots\dots$

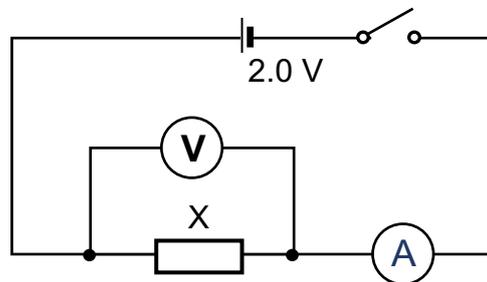- 4 The diagram below show a circuit that Jeanette uses to find the resistance of a resistor X. The e.m.f. of the cell E is 2.0 V and the voltmeter has a resistance of $2.5 \times 10^3 \text{ }\Omega$.



- (a) If the actual resistance of X is $2.0 \times 10^3 \text{ }\Omega$, and the resistance of the ammeter is much smaller than that of X, calculate
- (i) the reading of the ammeter, and
 - (ii) the value of the resistance of X that Jeanette gets.

ammeter reading = $\dots\dots\dots$

value of resistance of X obtained = $\dots\dots\dots$

- (b) Explain why the value of X obtained by Jeanette is different from the actual value.

$\dots\dots\dots$


$\dots\dots\dots$

$\dots\dots\dots$


$\dots\dots\dots$

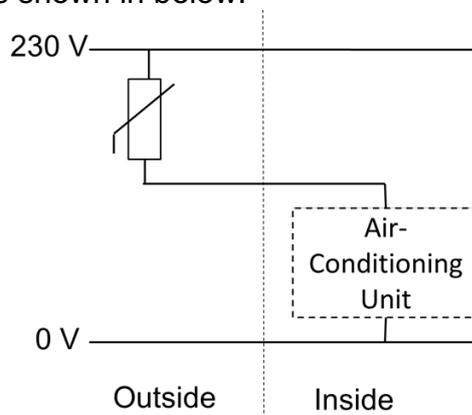- (c) In the space below, draw the correct circuit that she should connect to determine the value of X.

- 5 A thermistor is placed outside a room and is connected to an air-conditioning unit inside the room as shown in below.



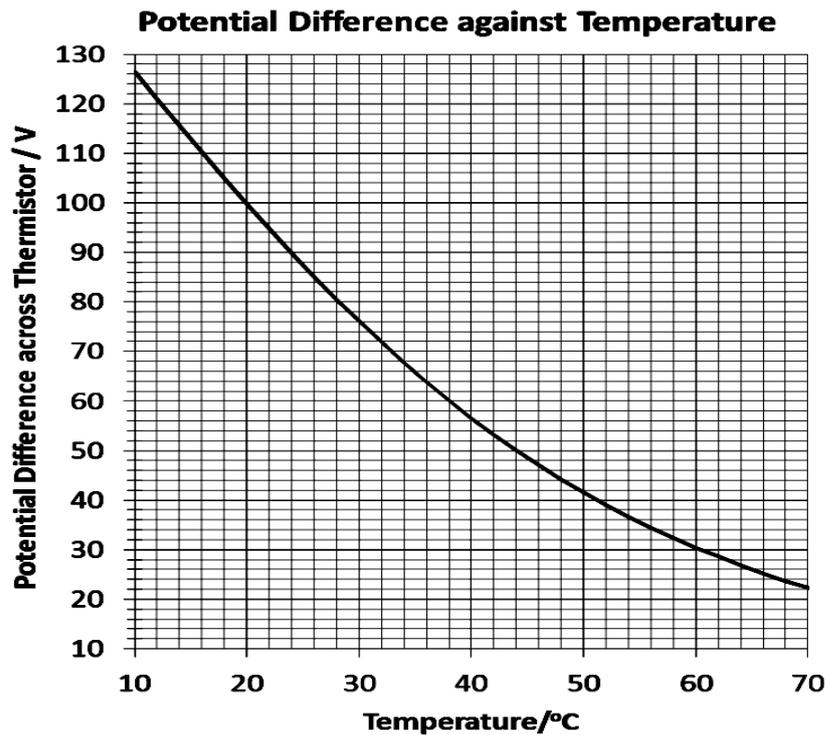The graph below shows how the potential difference across this thermistor changes with temperature.



- (a) State and explain what happens to the resistance of the thermistor as temperature increases.

.....
.....
.....

- (b) Using the diagrams above, state whether the potential difference across the air conditioning unit increases, decreases, or remains the same, when the temperature outside the room increases.

.....
.....

- (c) The air conditioning unit automatically switches on when the potential difference across it exceeds 154 V.

State the temperature at which the air-conditioning unit switches on.

temperature =

- (d) The resistance of the thermistor is 1630Ω when the temperature is 40°C . Assume that the resistance of the air-conditioning unit is fixed.

- (i) From the graph above, determine the potential difference across the thermistor when the temperature is 40°C .

potential difference =

- (ii) Calculate the current flowing through the thermistor when the temperature is 40°C .

current =

- (iii) Determine the potential difference across the air-conditioning unit when the temperature is 40°C .

potential difference =

(iv) Calculate the resistance of the air-conditioning unit.

resistance =

(e) Based on your answer in part (d) (iv), determine the resistance of the thermistor at 58°C.

resistance =

6 Fig. 1 below shows how the resistance of a thermistor varies with temperature.

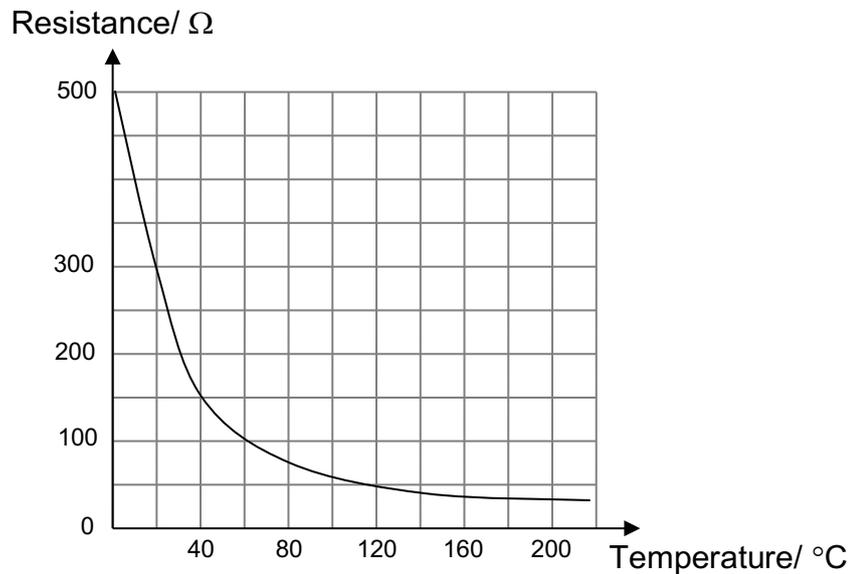


Fig. 1

(a) From the graph, what is the resistance of the thermistor at 80 °C?

resistance =

(b) A student connects the above thermistor in series with a 2.0 V dry cell and a 15.0 Ω resistor. The thermistor is then placed in a beaker of water kept at 80 °C. What is the current flowing through the circuit?

current =[2]

- (c) The same thermistor is removed from the beaker of water and then connected in series with a bulb of resistance $15.0\ \Omega$. They are then connected in parallel with a heating element of resistance $10.0\ \Omega$ as shown in **Fig. 11.2**. The heating element is placed close to the thermistor.

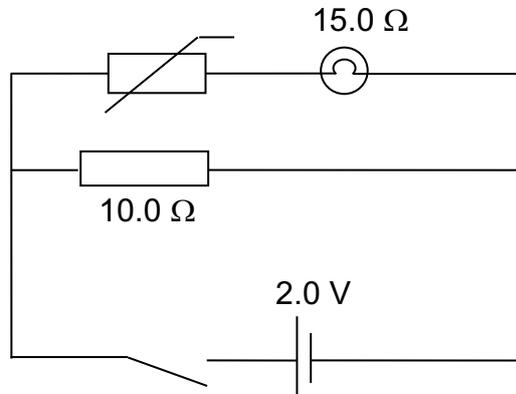


Fig. 11.2

- (i) When the switch is closed, it is observed that the bulb did not light up immediately. However, the bulb gradually lit after a short while later.
Explain these observations clearly.

.....

.....

.....

.....

.....

.....

- (ii) If the bulb barely lights up when a current of $12.1\ \text{mA}$ flows through it, what is the lowest temperature of the thermistor that would cause the bulb to light up?

lowest temperature =[3]