



2021 Sec 4 Physics Assignment 14

Current of Electricity - Answers

Reminders:

1. Use subscripts for similar quantities belonging to different components, e.g. R_1 , R_2 .
2. Write down the **basic formulae** before substitution.
3. Show all key mathematical steps clearly.
4. Evaluate your final answer!

AS 14

- 1 $I = Q / t$
Current in lightning = $120 \text{ C} / 0.20 \text{ s} = 600 \text{ A}$
- 2 (a) Current through Resistor A = $2 \times 0.5 \text{ A} = 1.0 \text{ A}$
Resistor A is connected in parallel to the path where point X lies. Point X lies along a path with 2 resistors. Therefore, the current through Resistor A will be twice that at X.
(b) Current through Resistor B = $0.5 \text{ A} + 1.0 \text{ A} = 1.5 \text{ A}$
Resistor B is in series with the battery, where the two paths (one with Resistor A and one with point X) converges.
- 3 $R = \rho L / A = \rho L / \pi r^2 = (7.0 \times 10^{-7} \times 600) / \pi (5.0 \times 10^{-4})^2$
 $= 534.76 \Omega$
 $= 530 \Omega$ (2 sf)
- 4 $R_y = 5.0 \Omega$
- 5 $R_x : R_y = 16 : 1$
 $= R_x / R_y = 16$
- 6 (a) Rheostat or variable resistor
(b) (i) 0.053 A
(ii) $R = V / I = 2.5 / 0.053 = 47 \Omega$ (2 sf)
(iii) $I = V / R = 2.5 / 200 = 0.013 \text{ A}$ (2 sf)
(iv) $I = 0.053 + 0.0125 = 0.066 \text{ A}$ (3d.p)