




NANYANG GIRLS' HIGH SCHOOL
2021 Sec 4 Physics Practical 02

Marking Scheme

Part 1 (total : 11 marks)


c) [1]

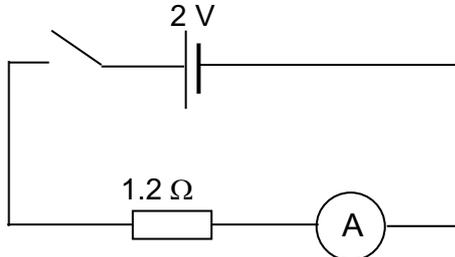

Precision of ammeter: 0.01 A

d) The value of I_1 should not be greater than 2 A (0.91 A) and must be in 2 d.p. [1]

f) [1]

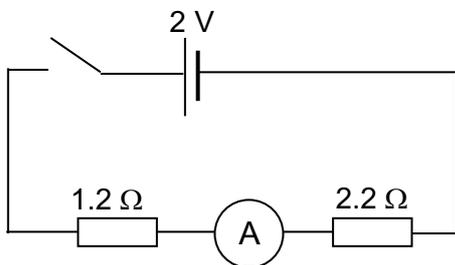

Precision of ammeter: 0.01 A

(if correct for both precisions)

g) The value of I_2 should not be greater than 1 A (0.6 A) and must be in 2 d.p. [1]

Questions


1 Current = $2.0 / 2.2 = 0.91$ A [1]

2 The calculated value I_1 is higher as the e.m.f. is divided by a lower total resistance of the circuit, where the internal resistance of the ammeter is assumed to be zero.

OR resistance of the wires were taken to be negligible. [1]

3 Move the existing ammeter to positions A_1 and A_2 as shown in the diagram and measure the current flowing through at those positions. The readings should be the same. [1]

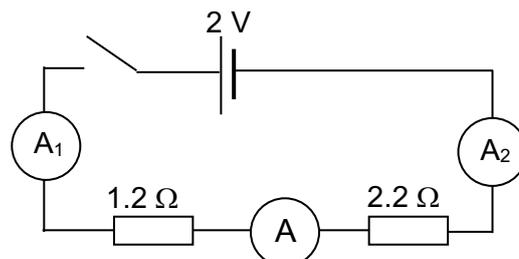The additional ammeters will increase the resistance of the circuit significantly because the resistance of the circuit is rather low.




[1]

4 Use a screwdriver or a coin to turn the screw attached to the ammeter needle in front until the error is corrected. [1]

- 5 Place your eye directly above the needle and adjust the position of the eye until the image of the pointer in the mirror coincides (or aligns) with the pointer. [1]

Part 2 (total: 9 marks)

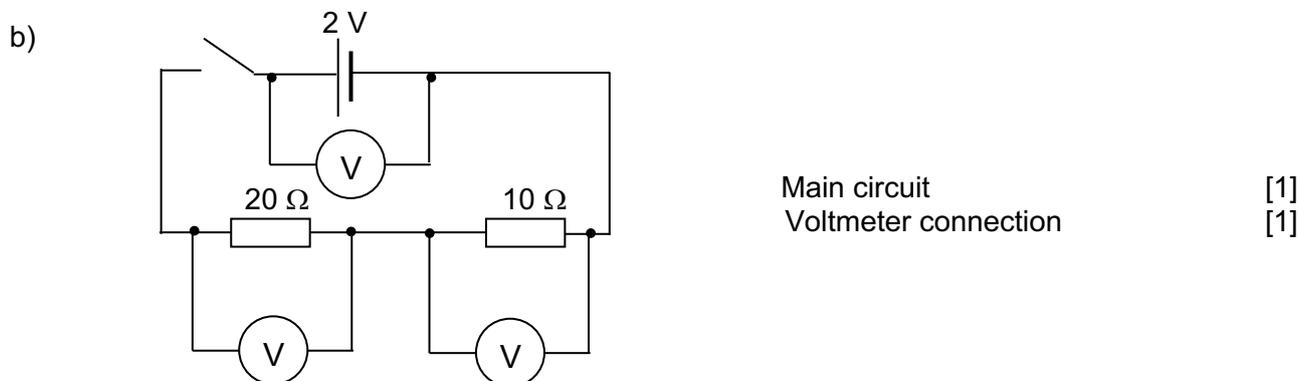- a) Precision of voltmeter = 0.05 V (half the smallest division) [1]



- c) V_{AB} , V_{BC} and V_{AC} must have a reading with correct 2 d.p.[1] and unit [1]

Note :

($V_{AB} + V_{BC}$) may not add up to V_{AC} due to experimental error like poor connections.

- e) Table of V_{AB} , V_{BC} and V_{AC} completed to correct 2d.p [1] and has NO units [1]

f) **Conclusion**

$$V_{AB} + V_{BC} = V_{AC}$$

[1]

OR

sum of p.d.s across the resistors in series = e.m.f. across accumulator
(or resistor+rheostat in series)

(Note : if the readings are not equal, the student must explain the reason)

Question

- 1 With the additional 2 V accumulator, the total e.m.f. of the circuit will increase to 4 V. When the voltmeter is used to measure V_{AC} , the needle will exceed its maximum deflection range (3 V). [1]

Note:

- e.m.f. = electromotive force
- e.m.f. across/of a accumulator/battery
- p.d. across a resistor/component
- **NOT** e.m.f. / p.d. passing through a component / circuit