



NANYANG GIRLS' HIGH SCHOOL
2021 Sec 4 Physics Practical 03

Marking Scheme (10 marks)

Note to teachers: Practical values may be quite different from theoretical values (the relationship where $\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2$ may not be obvious). Do **discuss theoretical values and underlying assumptions** (negligible resistance in resistors, ammeter, infinite resistance in voltmeter) in class.

Advice: Students to measure e.m.f. to ensure it is at least 2.70 V at the start of experiment.

Sample and theoretical values (in brackets)

$E = 2.90 \text{ V}$ (3.00 V)

	I	I₁	I₂
Fig. 1 (b & c)	0.48 A (0.90 A)	0.16 A (0.30 A)	0.30 A (0.60 A)
Fig. 2 (e)	0.34 A (0.60 A)	0 A (0 A)	0.34 A (0.60 A)
	<i>smaller than in Fig 1 since one 1 branch left</i>	<i>path through 10 Ω is broken</i>	<i>Same as in Fig 1, since same e.m.f. & R = 5 Ω</i>
Fig. 3 (f)	0.60 A (1.20 A)	0.15 A (0.30 A)	0.26 A (0.60 A)
	$\mathbf{I} = 2\mathbf{I}_1 + \mathbf{I}_2$	Same as Fig. 1	Same as Fig. 1

b) Precision = 0.01 A & **I** should not be greater than 0.90 A and must be in **2 d.p.** [1]

c) The value of **I₁** < 0.30 A (in **2 d.p.**) [1]

The value of **I₂** < 0.60 A (in **2 d.p.**) [1]

Relationship: $\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2$ [1]

d) The value of **E** > 2.70 V (in **2 d.p.**) $E = 2.90 \text{ V}$, [1]

The value of **V_{PQ}** could be < 2.00 V (in **2 d.p.**) $V_{PQ} = 2.00 \text{ V}$ [1]

e) $\mathbf{I} = \mathbf{I}_2$ (< 0.60 A) & $\mathbf{I}_1 = 0$ [1]

Comparing Fig 2 with Fig 1, **I** is smaller, **I₁** becomes zero, & **I₂** is slightly larger (or same). [1]

f) The value of **I** < 1.20 A, **I₁** < 0.30 A and **I₂** < 0.60 A. [1]
 (currents recorded in **2 d.p.**)

Comparing Fig 3 with Fig 1, **I** is larger, **I₁** & **I₂** remains the about the same. [1]