



NANYANG GIRLS' HIGH SCHOOL
2022 Sec 4 Physics Practical 03
Potential Difference and Current in a Resistor & a Filament Lamp

Suggested Markscheme

Record of measurements

- Table with wide vertical columns (*to record readings in table immediately*)
- Headings with units **I** / A, **V** / V, and $\frac{\mathbf{V}}{\mathbf{I}} / \text{VA}^{-1}$ or Ω (*last column for filament lamp only*)
- Acceptable values and correct d.p. for **I** and **V** (precisions: 0.01 A and 0.05 V)
- correctly calculated ratio and s.f. of $\frac{\mathbf{V}}{\mathbf{I}}$ (least s.f. of **V** and **I**, **2s.f.**) (*for resistor only*)
- Wide range (at least 0.3 A) and fairly well spread out values of **I**

Acronym to remember checklist for graph: **SPLACT**

Graph of V against I

- **S**cales are suitable, spaced out points
- **P**oints are correctly plotted: *plot different points if lines intersect*, e.g. “x” and “⊙”
- **L**ines are sharp/of uniform thickness
 - **Resistor: best fit line:** about equal no. of points on each side & points on each side are spaced out), not force line through origin
 - **Filament lamp:** smooth curve with about equal no. of points on each side, passing through origin
- **A**xes **V** against **I**, correct labelling, intersection labelled

Fig. 1: Fixed resistor

Gradient G

- **C**oordinates for the 2 points selected for gradient
 Large **T**riangle on graph for gradient ($\geq \frac{1}{2}$ length of line) }
- gradient of graph = $(y_2 - y_1) / (x_2 - x_1) \approx 0.45 \pm 0.05$

Conclusion

- I is directly proportional to V (if graph passes through or close to origin)
- fixed resistor obeys Ohm’s law.

OR V increases linearly as I increases (if graph does not pass through origin)

Fig. 2: Filament lamp

Conclusion

- I increases as V increases
- Filament lamp does not obey Ohm’s law

Questions

1. To ensure that the current is a minimum at the beginning. This will prevent a sudden surge of a large current flowing through the circuit which may damage circuit components, when the circuit is closed.
2. To prevent the heating effect of the current which would cause the resistance of circuit components to change and affect the V and I readings.
3. This may cause the voltmeter and the ammeter readings to fluctuate.
OR
This may increase the effective resistance of the circuit and hence affect the V and I readings.
4. $R = V / I$ is given by $(\text{gradient of graph})^{-1} \approx 2.2 \pm 0.2 \Omega$
5. The I-V graph for the resistor is a straight line passing through (or close to) the origin, indicating that it has a constant resistance.
The I-V graph for the filament lamp is a curve with decreasing gradient, indicating that its resistance decreases with increasing current (or p.d.).

Discussion

The statement is only true if the resistor is an ohmic conductor, as in the circuit in Fig.1.

By definition, the resistance is the ratio of V to I.